

ELECTRICAL CIRCUITS

Name: _____

Cell number: _____

E-mail address: _____

UNITS AND SYMBOLS

Potential difference (V)	Volt (V)	Charge (Q)	Coulomb (C)
Current strength (I)	Ampère (A)	Time (Δt)	Seconds (s)
Resistance (R)	Ohm (Ω)	Power (P)	Watt (W)
Labor (W) and Energy (E)	Joule (J)		


SUMMARY: LAWS AND DEFINITIONS

DEFINITIONS:	
Coulomb's law	The size of the electrostatic force that one point charge exercises onto another point charge is directly even to the product of the sizes of the charges and conversely even to the square of the distance between them.
Electrical field at a point	The electrostatic force experienced per unit's positive charge placed at that point.
Ohm's law	The potential difference over a conductor is directly even to the current through the conductor at a constant temperature.
WGK	The wgk-value of WS is the GS-potential difference/current that uses the same amount of energy as the WS.

	SERIES CIRCUIT	PARALLEL CIRCUIT
Current strength measured in Ampere (A) Symbol : I	I has the same value everywhere in the series circuit. $I_T = I_1 = I_2 = I_3$	The circuit in a parallel circuit splits into the 2 or more branches/ extensions (indirectly even to the size pf the resistance) (Current divider)
Potential difference measured in Volt (V) Symbol: V	The volt meter readings are added up to determine the total Volt meter reading of the series circuit. $V_T = V_1 + V_2 + V_3$ (Potential divider)	The volt meter readings remain the same for all the parallel branches in the circuit. $V_T = V_1 = V_2 = V_3$
Resistance measured in Ohm (Ω) Symbol: R	All the resistors in a series circuit must be added up to determine the total resistance of the series circuit. $R_T = R_1 + R_2 + R_3$	Here you have to calculate the equivalent resistance of a resistance in Series. $\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$

Important formulas:

Important:

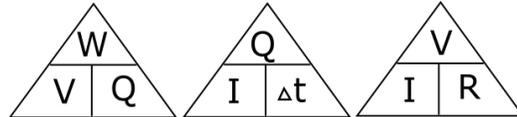

- **Current** is the pace at which charge flows.
- **Potential difference** is the labor done per unit positive charge. When 1 J energy is needed to move 1 coulomb charge between two points, there is a potential difference of 1 V ($V = \frac{W}{q}$).
- **Resistance** is a material's resistance against the flow of a current. When a conductor transmits a current of 1 A if there is a potential difference of 1 V over its points, the conductor has a resistance of 1 Ω ($\frac{V}{I} = R$). The **internal resistance** of the cell is the resistance presented against the flow of charge.
- An **Ohmic conductor** is one that obeys Ohm's law.
- A **Non-ohmic conductor** is one that disobeys Ohm's law.
- **Emk** is the total energy produced per coulomb charge through the cell ($V = \frac{W}{q}$).

IMPORTANT FACTS TO REMEMBER

- **Current in series** circuit is **the same everywhere**.
- If a **volt meter is connected over a parallel liaison** the volt meter fits with **every branch** and with the **total resistance** of the parallel liaison.
- The **resistance of a volt meter is very big** – does not allow any current flow.
- The **resistance of an ammeter is very small** – the main current always flows through.
- If **I = 0** and a **voltmeter makes contact with both poles** of the cell, **the volt meter reads the EMK of the cell**.
- If **current flows**, the **volt meter cannot take a reading over the cells**.
- **EMK is the maximum energy that the cell can deliver for every Coulomb charge**.
- The **bigger the resistance** in a circuit, the **smaller the current**.
- The **more cells connected in series**, the **bigger the total resistance**.
- The **more resistors connected in parallel**, the **smaller the total resistance**.

EMK AND INTERNAL RESISTANCE

In an open circuit the volt meter shows the emk.

In a closed circuit the volt meter reading decreases, the meter now shows V_{external} .

The difference between the two readings represents the tension over the internal resistance.

$$\text{Emk} = I(R+r)$$

The current in a circuit can be determined if:

A **resistor size** and the **potential difference** over the resistor is known ($\frac{V}{R} = I$).

The **internal resistance** and **internal tension** is known ($\frac{V_{\text{intern}}}{r} = I$).

All **resistor sizes** and the **emk** is known ($\frac{\text{emk}}{R_{\text{tot}} + r} = I$).

The **total external resistance** and **potential difference** over the battery is known ... ($\frac{V_{\text{eks}}}{R_{\text{tot}}} = I$).

